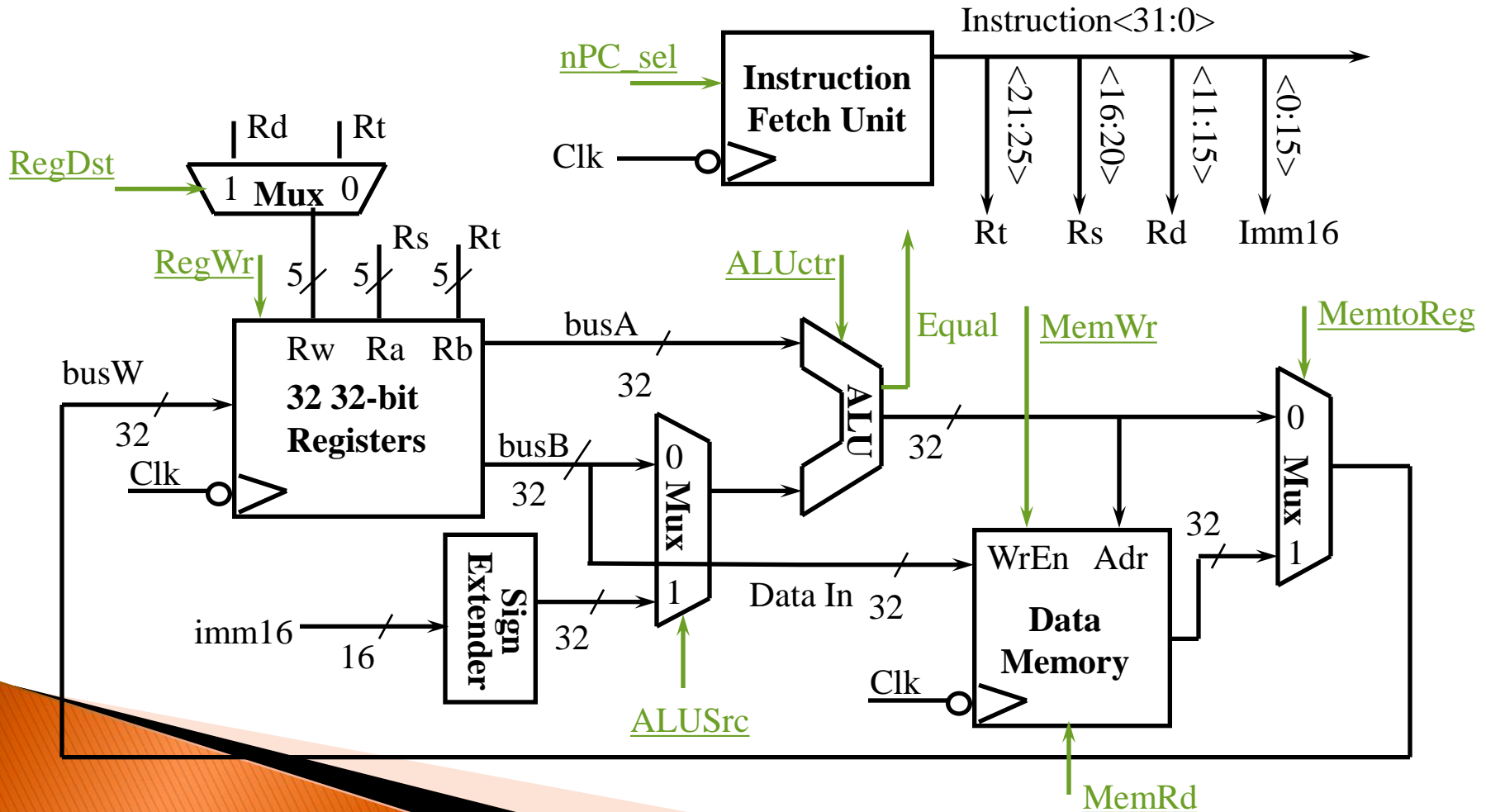


CSE331 – Computer Organization


Lecture 7: Single Cycle Control

A Single Cycle Datapath

- ▶ We have everything except control signals (underlined)
 - Today's lecture will look at how to generate the control signals



RTL: R-Type Instructions

 


► Example: `add rd, rs, rt`


- `Mem[PC]` Fetch the instruction from memory
- $R[rd] \leftarrow R[rs] + R[rt]$ The actual operation
- $PC \leftarrow PC + 4$ Calculate the next instruction's address

Instruction Fetch Unit at the Beginning of Add

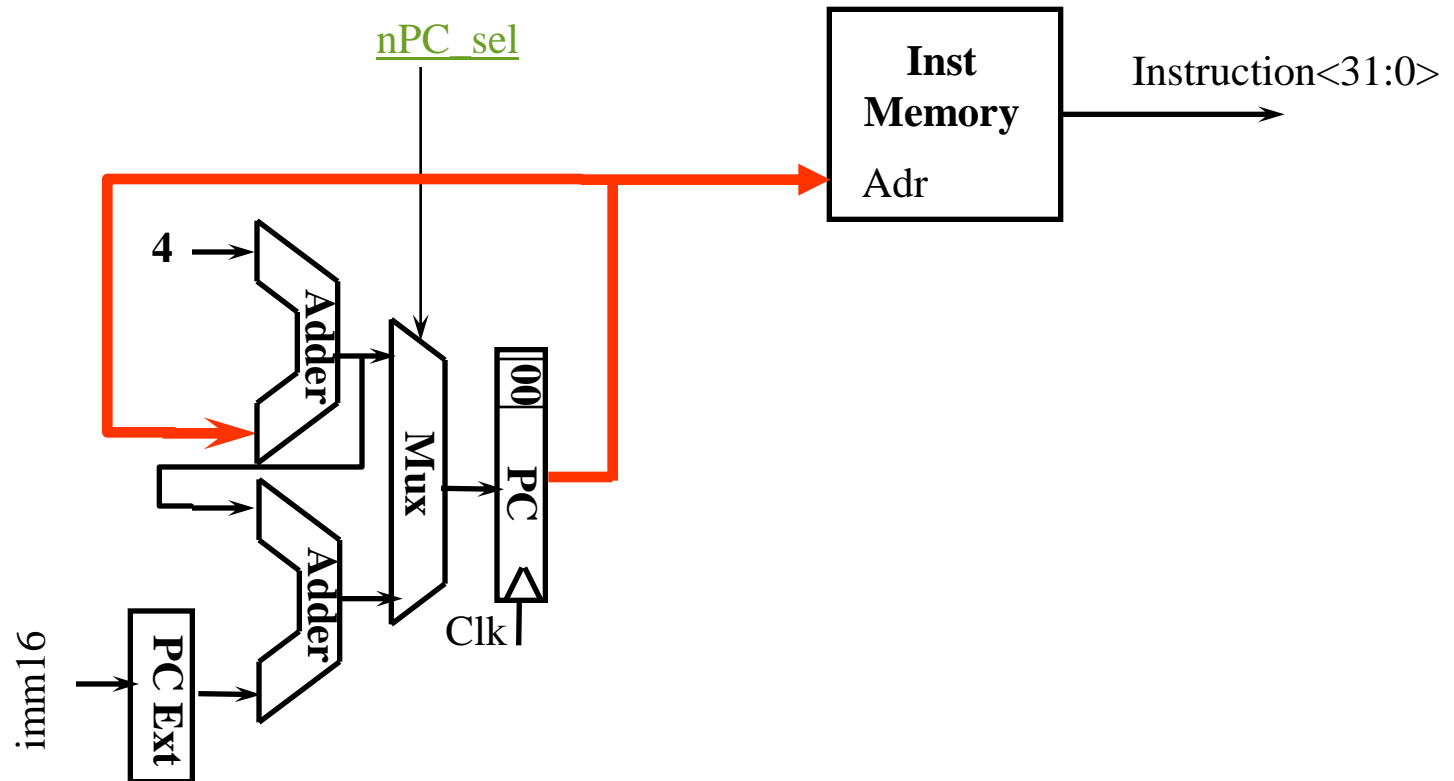
- Fetch the instruction from Instruction memory:
 $\text{Instruction} \leftarrow \text{mem}[\text{PC}]$
- Done for all instructions => Don't need special control bits



The Single Cycle Datapath during Add

 


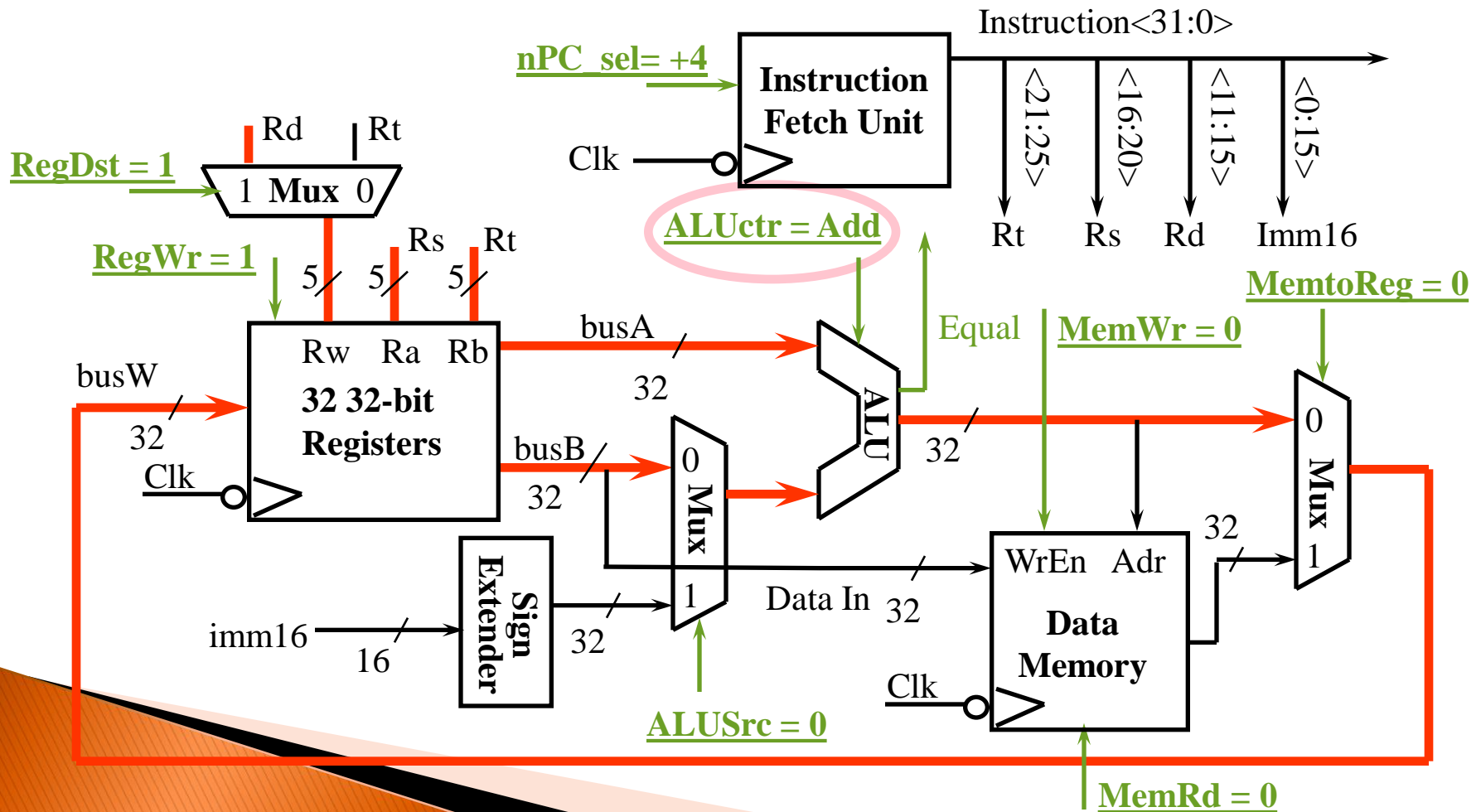► $R[rd] \leftarrow R[rs] \text{ op } R[rt]$




Instruction Fetch Unit at the End of Add

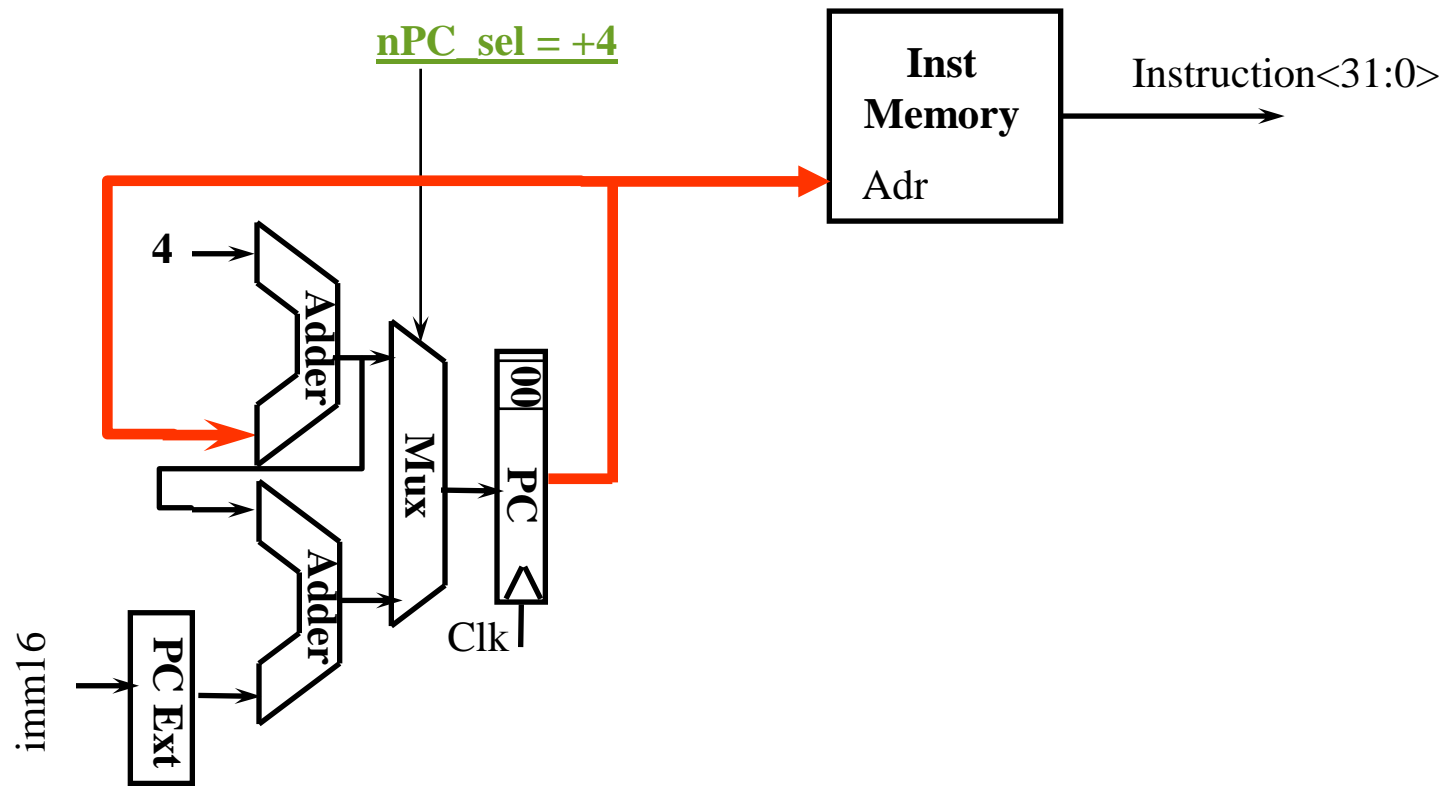
- ▶ $PC \leftarrow PC + 4$
 - This is the same for all instructions except Branch and Jump




The Single Cycle Datapath during Load

 

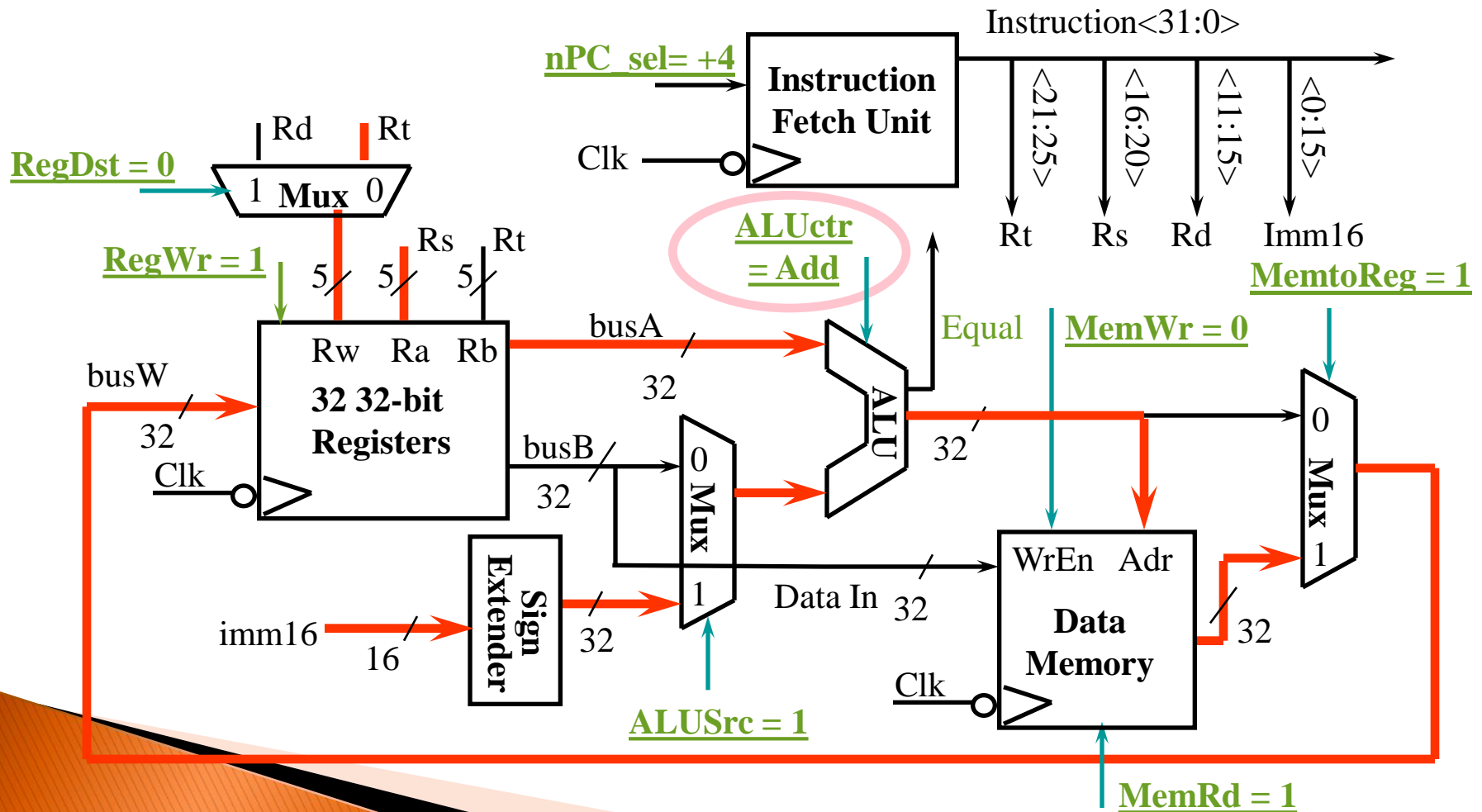
- ▶ $R[rt] \leftarrow \text{Data Memory } \{R[rs] + \text{SignExt}[imm16]\}$




The Single Cycle Datapath during Store

 

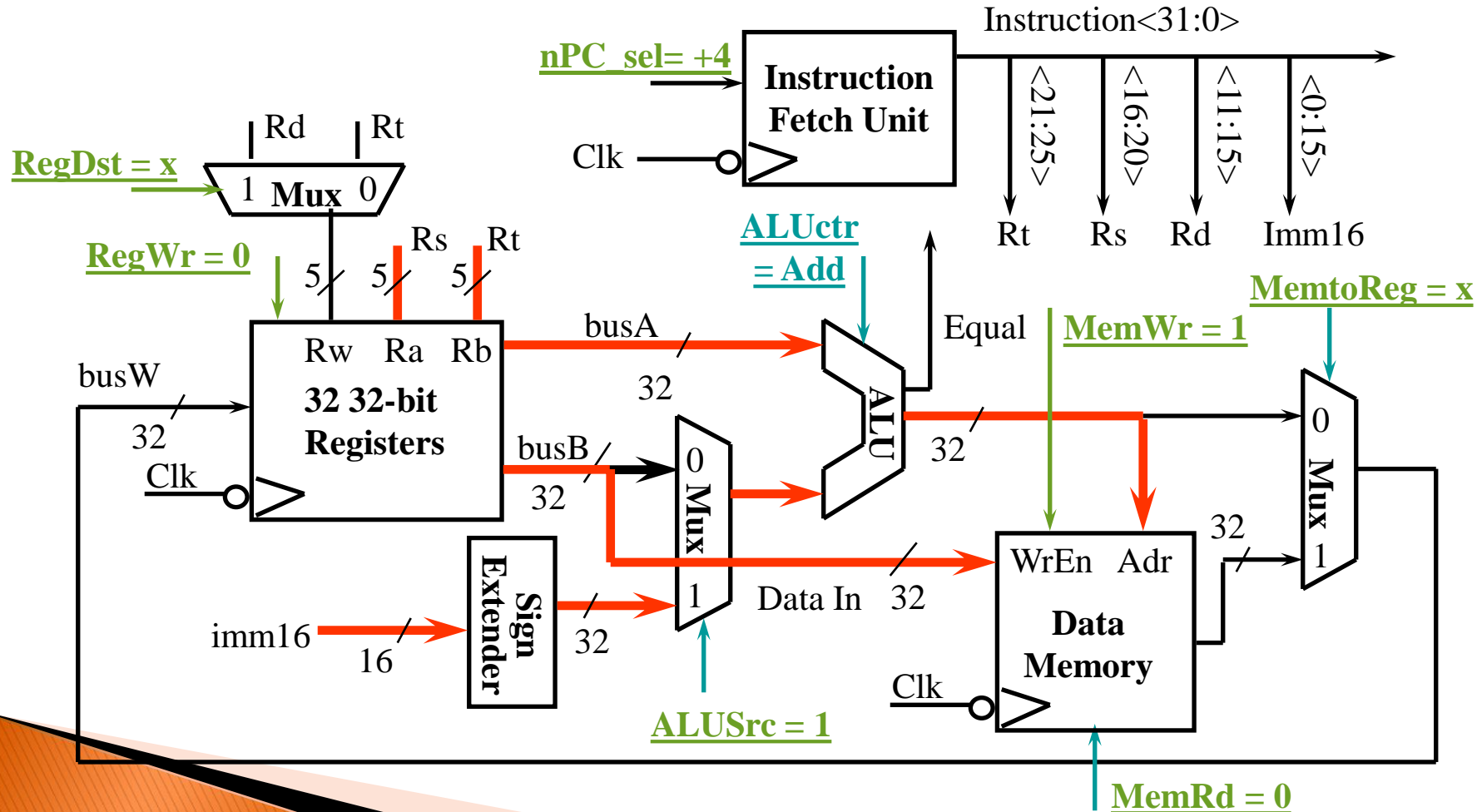
- ▶ Data Memory $\{R[rs] + \text{SignExt}[imm16]\} \leftarrow R[rt]$




The Single Cycle Datapath during Branch

 

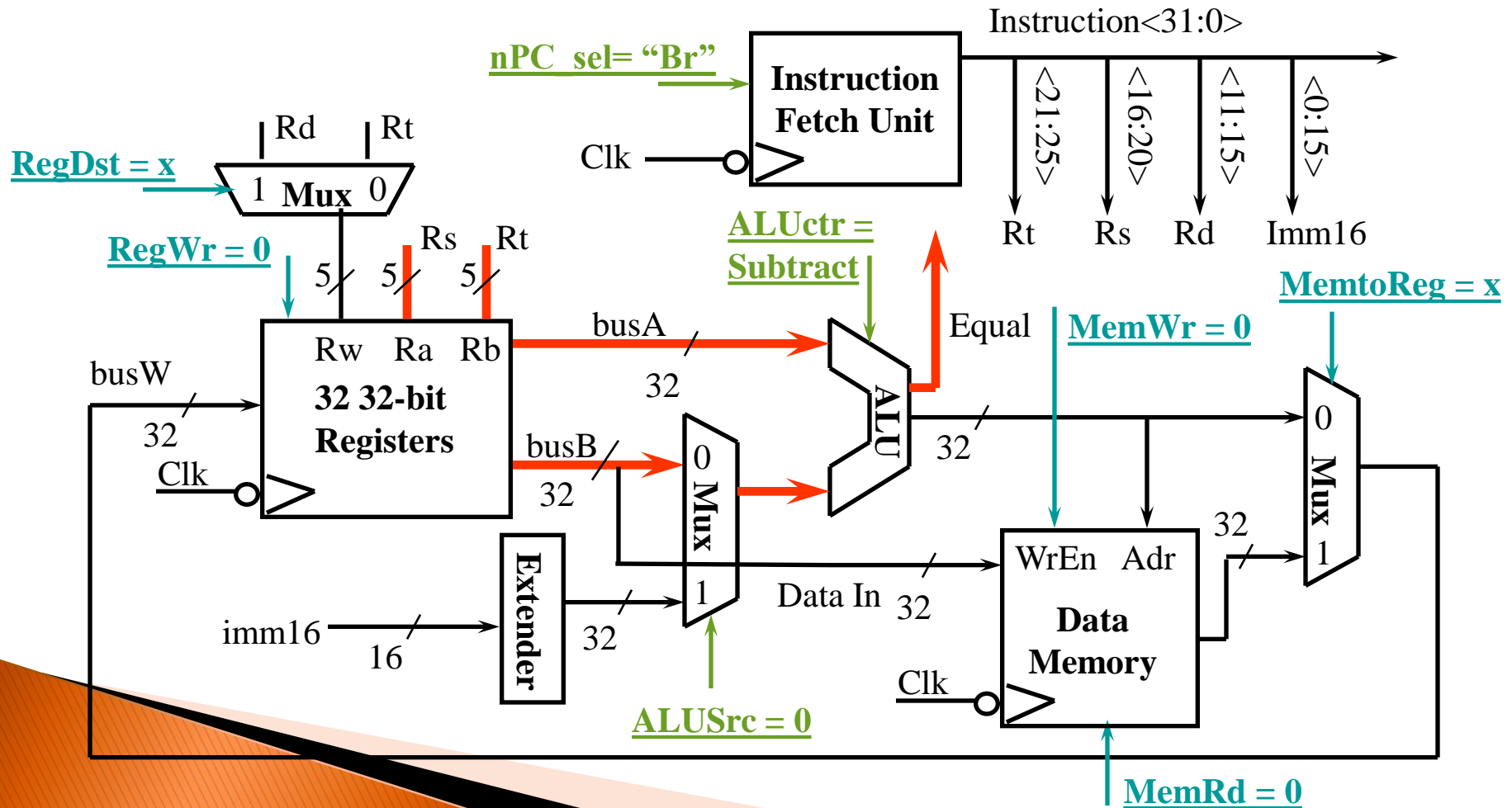
- ▶ if $(R[rs] - R[rt] == 0)$ then $Equal \leftarrow 1$; else $Equal \leftarrow 0$



 
Instruction Fetch Unit at the End of Branch



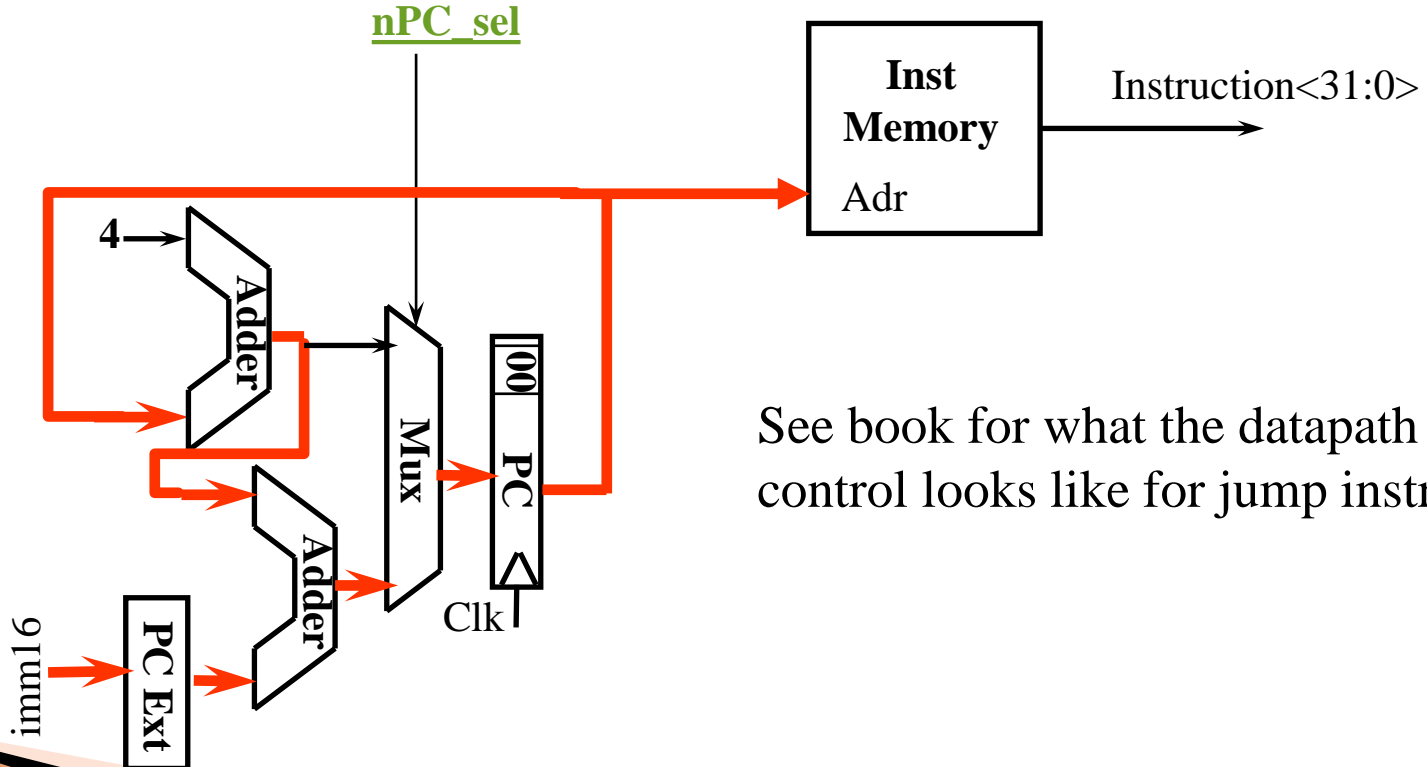- if (Equal & Branch)
then $PC = PC + 4 + \text{SignExt}[\text{imm16}] * 4$;
else $PC = PC + 4$



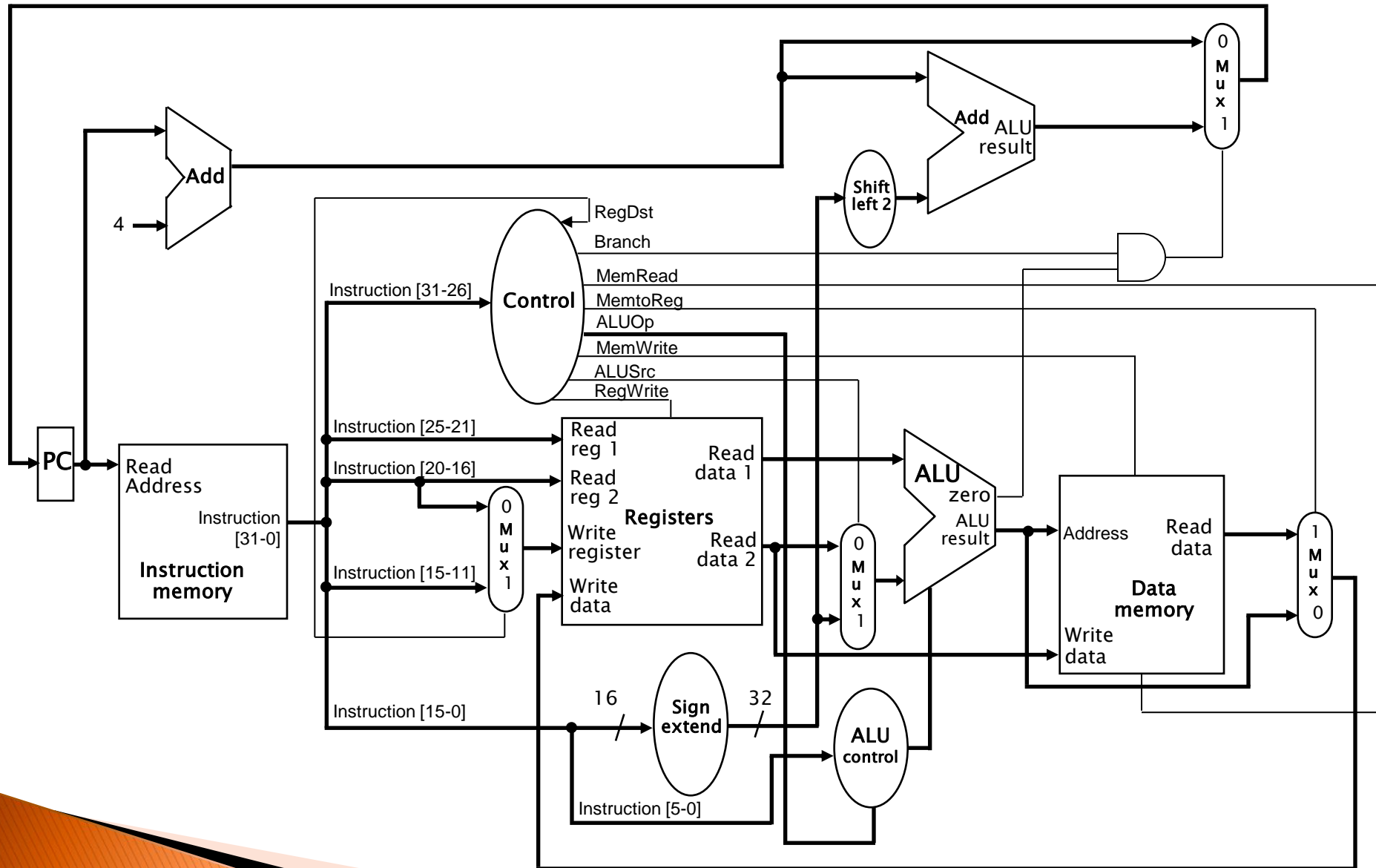Different View of Same Implementation (From Book)




Step 4: Given Datapath: RTL \rightarrow Control

Instr.	Reg Des	ALUSrc	Memto Reg	Reg Wr	Mem Rd	Mem Wr	Branch	ALUop1	ALUop0
R-type	1	0	0	1	0	0	0	1	0
lw	0	1	1	1	1	0	0	0	0
sw	X	1	X	0	0	1	0	0	0
beq	X	0	X	0	0	0	1	0	1

Table: Control Lines Determined by the opcode

ALU Control Bits

Instruction opcode	ALUop	Instruction operation	Function field	Desired ALU action	ALU control
LW	00	load word	XXXXXX	add	010
SW	00	store word	XXXXXX	add	010
beq	01	branch equal	XXXXXX	subtract	110
R-type	10	add	100000	add	010
R-type	10	subtract	100010	subtract	110
R-type	10	AND	100100	and	000
R-type	10	OR	100101	or	001
R-type	10	set on less than	101010	set on less than	111

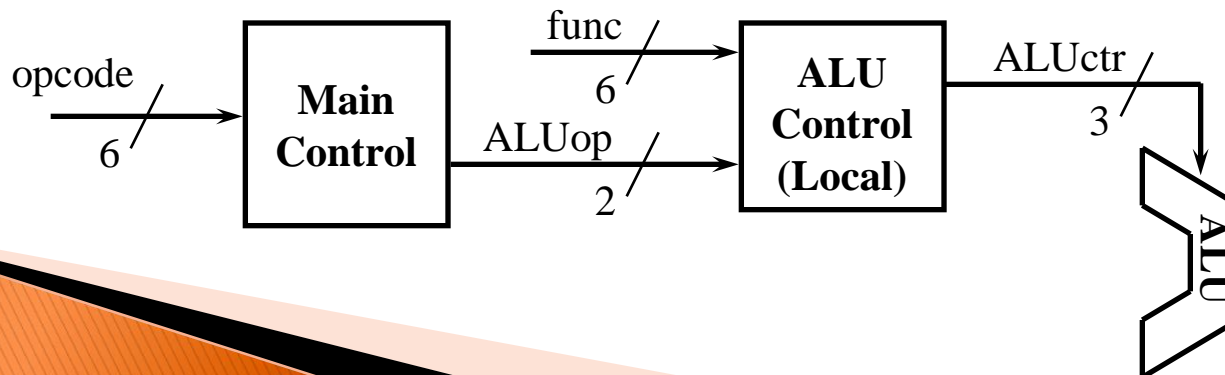

The Truth Table for the 3 ALU Control Bits

ALUop		Function filed						Operation
ALUop1	ALUop0	F5	F4	F3	F2	F1	F0	
0	0	X	X	X	X	X	X	010
0	1	X	X	X	X	X	X	110
1	0	1	0	0	0	0	0	010
1	0	1	0	0	0	1	0	110
1	0	1	0	0	1	0	0	000
1	0	1	0	0	1	0	1	001
1	0	1	0	1	0	1	0	111

func<5:0>	Instruction Operation
10 0000	add
10 0010	subtract
10 0100	and
10 0101	or
10 1010	set-on-less-than

The Logic Equation for ALUctr<2>

ALUop		Function filed						Operation
ALUop1	ALUop0	F5	F4	F3	F2	F1	F0	
0	0	X	X	X	X	X	X	010
0	1	X	X	X	X	X	X	110
1	0	1	0	0	0	0	0	010
1	0	1	0	0	0	1	0	110
1	0	1	0	0	1	0	0	000
1	0	1	0	0	1	0	1	001
1	0	1	0	1	0	1	0	111

▶ $ALUctr<2> = ALUop0 + (ALUop1 \& func<1>)$

The Logic Equation for ALUctr<1>

ALUop		Function filed						Operation
ALUop1	ALUop0	F5	F4	F3	F2	F1	F0	
0	0	X	X	X	X	X	X	010
0	1	X	X	X	X	X	X	110
1	0	1	0	0	0	0	0	010
1	0	1	0	0	0	1	0	110
1	0	1	0	0	1	0	0	000
1	0	1	0	0	1	0	1	001
1	0	1	0	1	0	1	0	111


▶ $\text{ALUctr}<1> = !\text{ALUop1} + !\text{func}<2>$

The Logic Equation for ALUctr<0>

ALUop		Function filed						Operation
ALUop1	ALUop0	F5	F4	F3	F2	F1	F0	
0	0	X	X	X	X	X	X	010
0	1	X	X	X	X	X	X	110
1	0	1	0	0	0	0	0	010
1	0	1	0	0	0	1	0	110
1	0	1	0	0	1	0	0	000
1	0	1	0	0	1	0	1	001
1	0	1	0	1	0	1	0	111


- $ALUctr<0> = ALUop1 \& (func<3> + func<0>)$

The ALU Control Block

 

- ▶ $ALUctr<2> = ALUOp0 + (ALUOp1 \& func<1>)$
- ▶ $ALUctr<1> = !ALUOp1 + !func<2>$
- ▶ $ALUctr<0> = ALUOp1 \& (func<3> + func<0>)$

The “Truth Table” for the Main Control

 


opcode	000000	100011	101011	000100
	R-type	lw	sw	beq
RegDst	1	0	x	x
ALUSrc	0	1	1	0
MemtoReg	0	1	x	x
<u>RegWrite</u>	<u>1</u>	<u>1</u>	<u>0</u>	<u>0</u>
MemRead	0	1	0	0
MemWrite	0	0	1	0
Branch	0	0	0	1
ALUOp (Symbolic)	“R-type”	Add	Add	Subtract
ALUOp1	1	0	0	0
ALUOp0	0	0	0	1


The “Truth Table” for RegWrite

opcode	00 0000	10 0011	10 1011	00 0100
	R-type	lw	sw	beq
RegWrite	1	1	0	0


- RegWrite = R-type + lw
 - = $\neg \text{op}\langle 5 \rangle \ \& \ \neg \text{op}\langle 4 \rangle \ \& \ \neg \text{op}\langle 3 \rangle \ \& \ \neg \text{op}\langle 2 \rangle \ \& \ \neg \text{op}\langle 1 \rangle \ \& \ \neg \text{op}\langle 0 \rangle$ (R-type)
 - + $\text{op}\langle 5 \rangle \ \& \ \neg \text{op}\langle 4 \rangle \ \& \ \neg \text{op}\langle 3 \rangle \ \& \ \neg \text{op}\langle 2 \rangle \ \& \ \text{op}\langle 1 \rangle \ \& \ \text{op}\langle 0 \rangle$ (lw)

 


Implementation of the Main Control

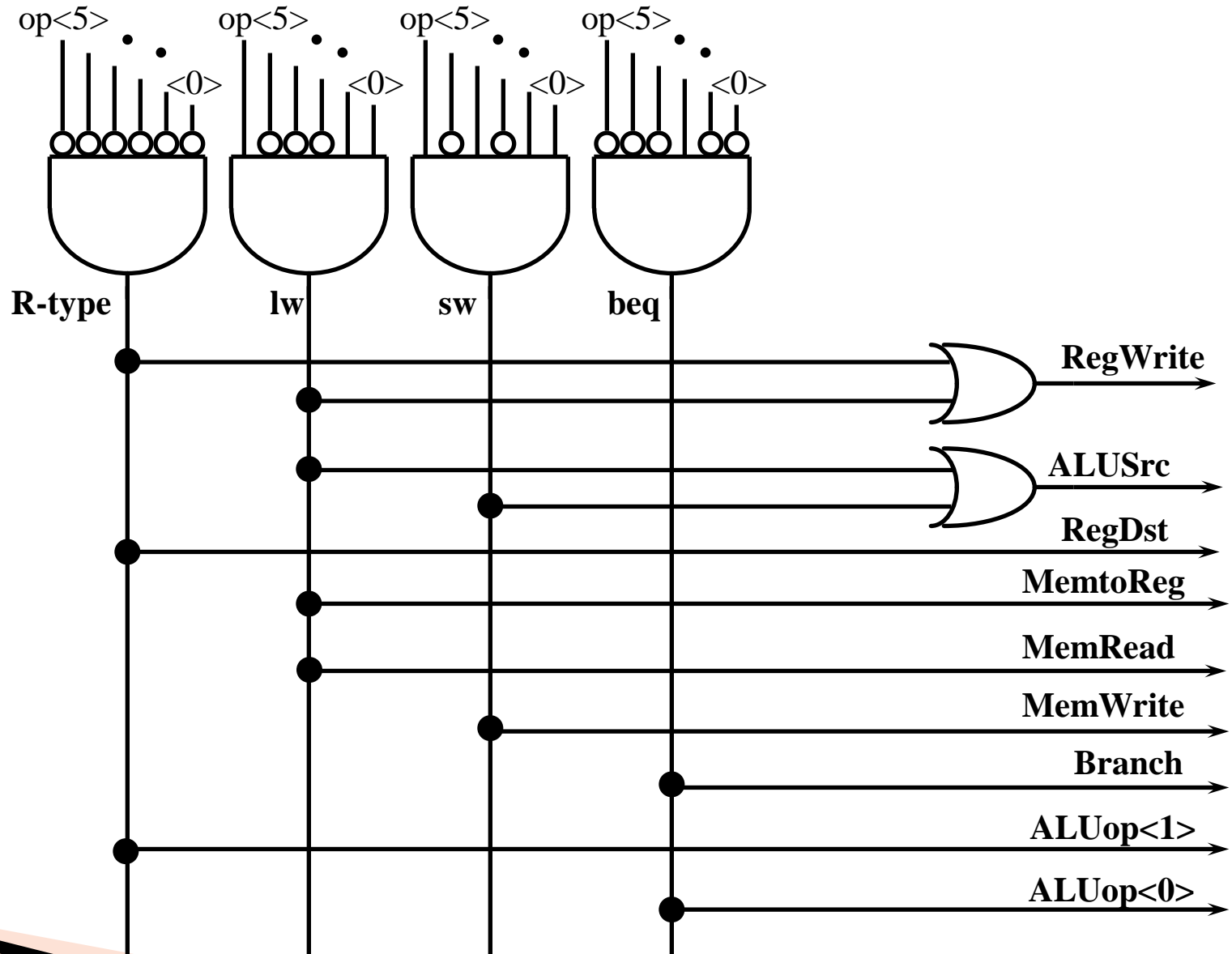

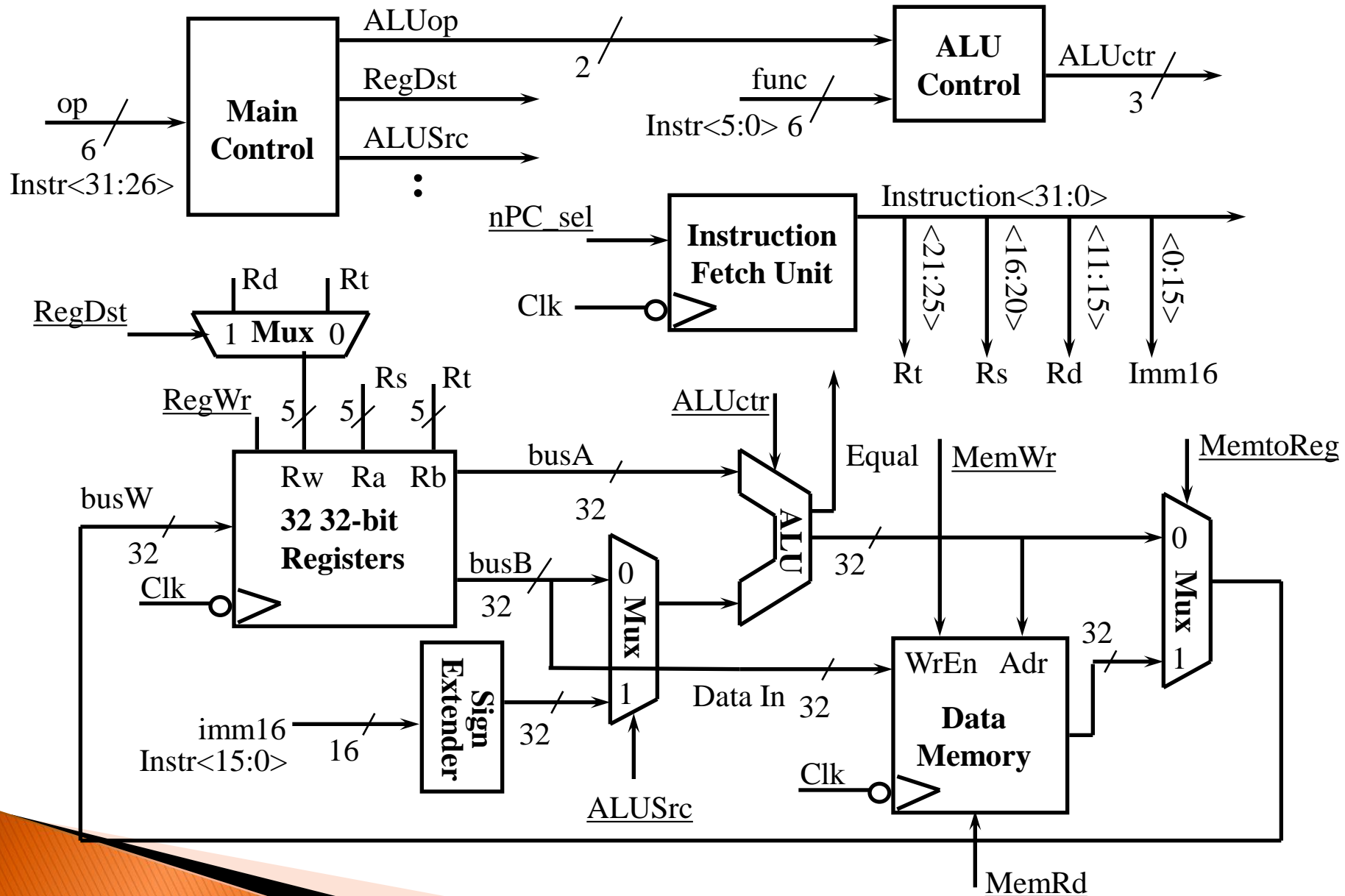Putting it All Together: A Single Cycle Processor



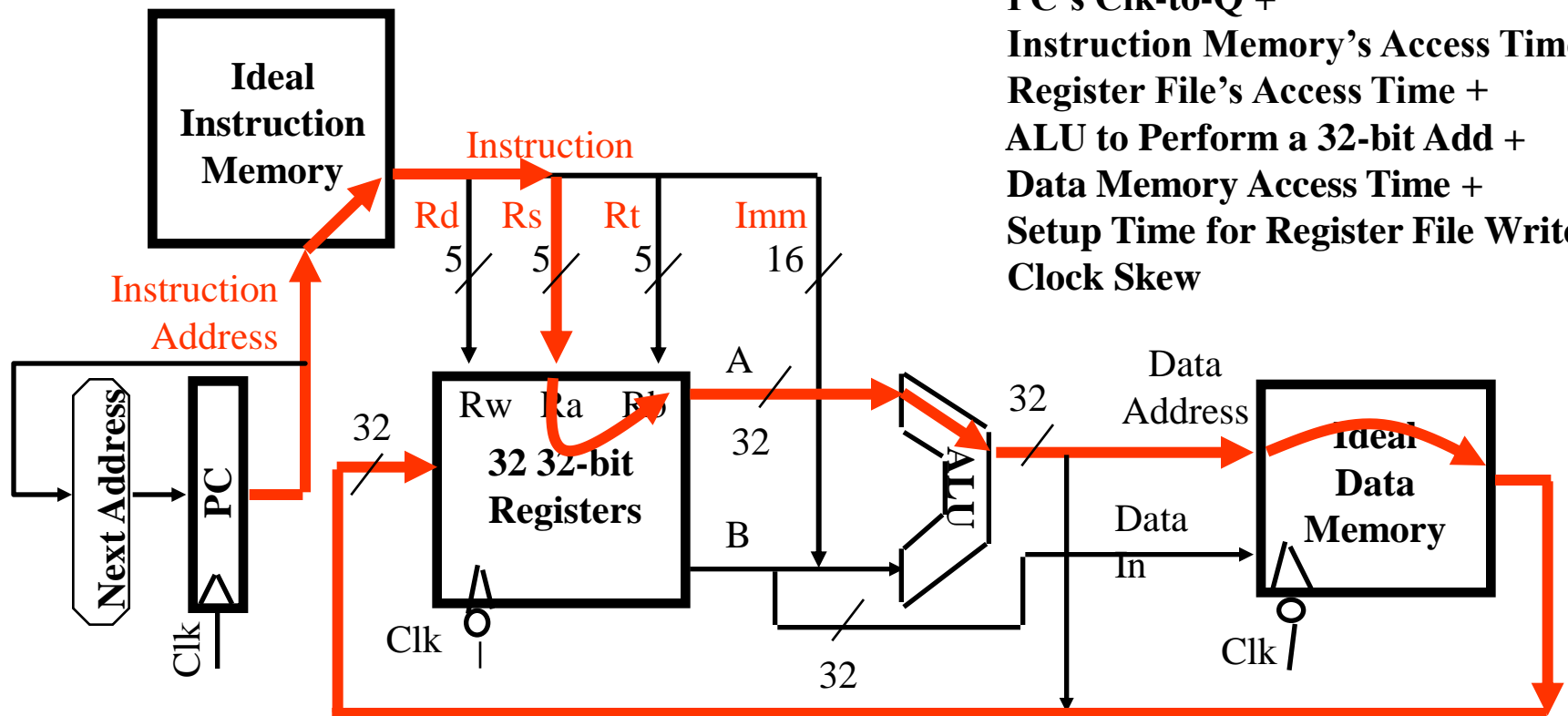An abstract view of the critical path – load instruction



Critical Path (Load Operation) =
PC's Clk-to-Q +
Instruction Memory's Access Time +
Register File's Access Time +
ALU to Perform a 32-bit Add +
Data Memory Access Time +
Setup Time for Register File Write +
Clock Skew

Worst case delay for load is much longer than needed for all other instructions, yet this sets the cycle time.